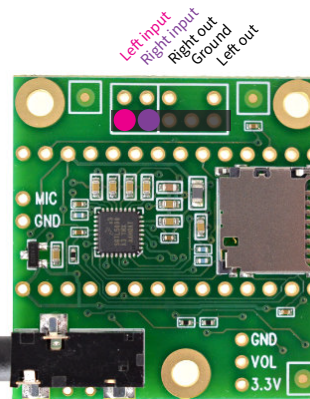


Class 5 - Audio In

The mic input can be used for most types elements.
Piezo, dynamic, ecrete, or even a small speaker work fine



Connect the pink dots together
with a jumer wire for a mono audio input
For stereo connect both the pink and purple

The 1/8" jack can be placed anywhere on the breadboard

