Class 5 - Audio In

Note that there was an error on the previous setup. You can't use A0

The mic input can be used for most types elements. Piezo, dynamic, ecrete, or even a small speaker work fine



Connect the pink dots together with a jumer wire for a mono audio input For stereo connect both the pink and purple

The 1/8" jack can be placed anywhere on the breadboard

